# **VLSI DESIGN**

### **FINAL PROJECT**

NAME : LOKESH R

ROLL NO : 711623106027

PROJECT TITLE: TRAFFIC LIGHT CONTROLLER WITH PEDESTRAIN SIGNAL.

**BOARD FAMILY: SPARTAN7** 

## 1,Design sorce


```
module traffic_light_controller(
  input wire clk,
  input wire reset,
  input wire pedestrian_request,
  output reg [2:0] traffic_light,
  output reg pedestrian_light
);
  localparam GREEN = 2'b00;
  localparam YELLOW = 2'b01;
  localparam RED = 2'b10;
  reg [1:0] state, next_state;
  reg [3:0] timer;
  reg pedestrian_waiting;
  always @(posedge clk or posedge reset) begin
    if (reset) begin
state <= GREEN;
       timer <= 0;
       pedestrian_waiting <= 0;
    end else begin
```

```
if (pedestrian_request)
       pedestrian_waiting <= 1;</pre>
    if (state == RED && timer >= 10)
       pedestrian_waiting <= 0;</pre>
    if (state != next_state)
      timer <= 0;
    else
       timer <= timer + 1;
    state <= next_state;
  end
end
  always @(*) begin
  case (state)
    GREEN: next_state = (timer >= 10) ? YELLOW: GREEN;
    YELLOW: next_state = (timer >= 3) ? RED : YELLOW;
    RED: next_state = (timer >= 10) ? GREEN : RED;
    default: next_state = GREEN;
  endcase
end
  always @(*) begin
  case (state)
    GREEN: begin
      traffic_light = 3'b001;
       pedestrian_light = 0;
    end
    YELLOW: begin
```


```
traffic_light = 3'b010;
         end
       RED: begin
         traffic_light = 3'b100;
         pedestrian_light = (pedestrian_waiting) ? 1:0;
       end
       default: begin
         traffic_light = 3'b001;
         pedestrian_light = 0;
       end
    endcase
  end
endmodule
2, SIMULATION SOURCE
`timescale 1ns / 1ps
module tb_traffic_light_controller;
  reg clk;
  reg reset;
  reg pedestrian_request;
  wire [2:0] traffic_light;
  wire pedestrian_light;
  traffic_light_controller uut (
    .clk(clk),
     .reset(reset),
     .pedestrian_request(pedestrian_request),
    .traffic_light(traffic_light),
    .pedestrian_light(pedestrian_light)
  );
```

```
initial begin
    clk = 0;
    forever #5 clk = ~clk;
  end
  initial begin
    reset = 1;
    pedestrian_request = 0;
    #20 reset = 0;
    #100;
    pedestrian_request = 1;
    #10 pedestrian_request = 0;
    #200;
    pedestrian_request = 1;
    #10 pedestrian_request = 0;
    #300;
    $stop;
  end
  initial begin
    $monitor("Time=%0t | Traffic Light={R,Y,G}=%b | Pedestrian=%b",
          $time, traffic_light, pedestrian_light);
  End
endmodule
```

#### 3, RTL ANALSYS

 


# 4, simulation

 


# 5, synthesis


#### 5.1 chamatic:

 

#### 5.2 Divice

 


# 5.3 Graph

 


## 6, Synthesis report

#### 6.1 Power:

 

#### 6.2 Utilization

 

## 7,Implementation

